

## Lecture 19, Mar 2, 2022

### Norton Equivalent Circuit

- The Norton Equivalent Circuit is the dual of the Thevenin Equivalent Circuit; instead of a voltage source in series with a resistor, in a Norton Equivalent Circuit the elements are replaced by a current source in parallel with a resistor
  - Thevenin and Norton circuits can be transformed into each other via source transformation
  - The Norton resistance is the same as the Thevenin resistance:  $R_N = R_{Th}$
  - The Norton current can be obtained by  $I_N = \frac{V_{Th}}{R_{Th}}$  via source transformation
  - Alternatively, short the terminals, and then  $I_N$  is the current flowing through this short
- If using a short circuit to find the Norton current, the direction of the current source must *complete the loop* with the short circuit current